

## Network Theorems

### Thévenin's theorem

→ This theorem is most extensively used theorem. It is applicable where it is desired to determine the current through or voltage across any one element in a network without going through the method of solving a set of network equations.

#### Statement

"Any two terminal bilateral linear dc circuit can be replaced by an equivalent circuit consisting of a voltage source and a series resistor."




A more general statement of Thévenin's theorem is that any linear active network consisting of independent and dependent voltage sources and current sources and linear bilateral network elements can be replaced by an equivalent circuit consisting of a voltage source in series with a resistance.

The voltage source being the open circuited voltage across the open circuited load terminals and the resistance being


the internal resistance of the source network looking through the open circuited load terminals.

### Explanation

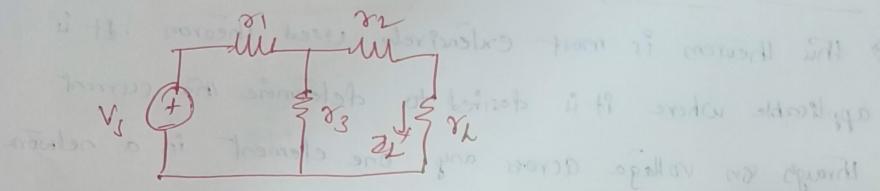

Let us consider a simple dc circuit as shown in fig. We have to find  $\mathcal{R}_L$  by Thévenin's theorem.

To find  $V_{oc}$

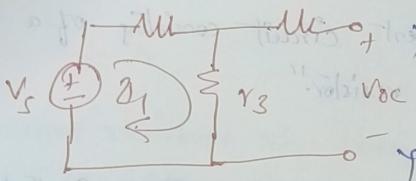


To find  $V_{oc}$ , open circuit the load terminals at which we calculate  $\mathcal{R}_L$ . And calculate open circuit voltage at load terminals which is equal to Thévenin voltage  $V_{th}$ .

$$V_{oc} = V_s \times \frac{R_3}{R_3 + R_2}$$

As load terminals are open circuited the current through  $R_2$  is zero.  
 $\therefore \mathcal{R}_L = 0$ .


To find  $R_{th}$

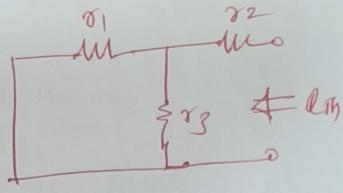To find internal resistance [Thévenin resistance (or) equivalent resistance] in series with  $V_{th}$ , the voltage source is removed by short circuit / current source removed for open circuit.



$$R_{th} = R_2 + \frac{R_1 R_3}{R_1 + R_3}$$

Equivalent Circuit

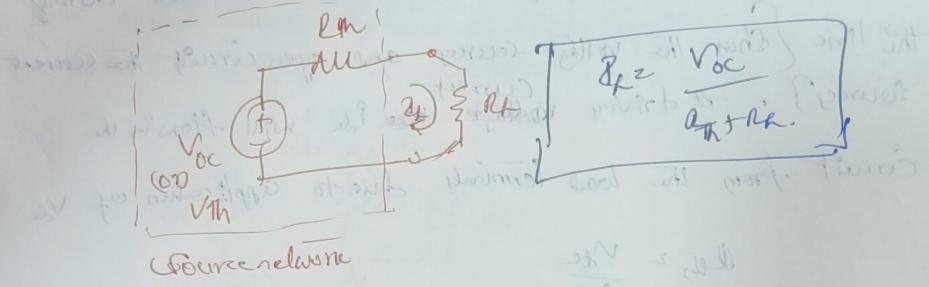

→ Internal resistance of voltage source is zero.

→ Internal resistance of current source is infinity

→ To find  $R_{th}$  for the circuits containing dependent sources  
in addition to  $V_{th}$  is absence of independent sources.

### BAT Method

Find  $V_{oc}$  across the open circuited terminals by conventional network analysis. Short the load terminals and find the short circuit current ( $I_{sc}$ ) through the shorted terminals.

The internal resistance of the network is obtained as

$$R_{th} = \frac{V_{oc}}{I_{sc}}$$

### 2nd Method

Remove the load terminals resistance and apply a dc driving voltage  $V_{dc}$  at the open circuited load terminals.

Keep the other independent sources deactivated during this time [short the voltage sources and open circuit the current sources]. A driving current  $I_{dc}$  will flow in the circuit from the load terminals due to application of  $V_{dc}$ .

$$R_{th} = \frac{V_{dc}}{I_{dc}}$$

Method 2: Short the load terminals & apply a dc voltage  $V_{dc}$  at the open circuited load terminals. The driving current  $I_{dc}$  will flow in the circuit from the load terminals due to application of  $V_{dc}$ .

Method 3: Open the load terminals & apply a dc voltage  $V_{dc}$  at the open circuited load terminals. The driving current  $I_{dc}$  will flow in the circuit from the load terminals due to application of  $V_{dc}$ .

$$I_{th} = \frac{V}{R_{th}}$$

$$I_{th} = \frac{V}{R_{th}}$$


Section - I Q. 1 state and explain superposition theorem.

### Superposition Theorem

6M

"In any linear bilateral circuit the response through an element is equal to the algebraic sum of the responses caused by each source acting at a time while all the

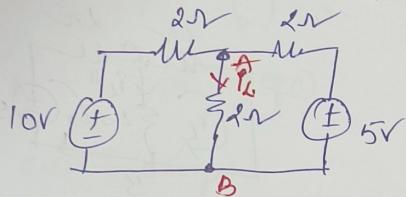{ Other sources are replaced by their internal impedances.  
i.e. Voltage sources replaced by short circuit Current sources replaced by open circuit ]  
let us consider an example




To find current  $i_x$  at AB Terminals

1. When 10V source is acting alone and  $v_d = 0$ .

Apply KVL in loop ①

$$-10 + 2i_1 + 2[i_1 - i_2] = 0.$$
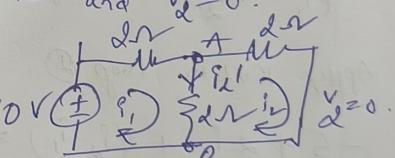
$$4i_1 - 2i_2 = 10 \rightarrow \text{eq } ①$$



Apply KVL in loop ②

$$2(i_2 - i_1) + 2i_2 = 0.$$

$$-2i_1 + 4i_2 = 0 \rightarrow \text{eq } ②$$

$$\begin{bmatrix} 4 & -2 \\ -2 & 4 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} 10 \\ 0 \end{bmatrix}$$

$$i_1 = \frac{A_1}{\Delta}$$

$$i_2 = \frac{A_2}{\Delta}$$

$$\Delta_1 = \begin{vmatrix} 10 & -2 \\ -2 & 4 \end{vmatrix} \quad A = \begin{vmatrix} 4 & -2 \\ -2 & 4 \end{vmatrix} \quad \Delta_2 = \begin{vmatrix} 4 & 10 \\ -2 & 0 \end{vmatrix}$$

$$\Delta_1 = [40 + 0] = 40 \quad \Delta_2 = [0 + 20] = 20.$$

$$I_1' = \frac{\Delta_1}{A} = \frac{40}{12} = \frac{10}{3} \quad A = [16 - 4] = 12$$

$$I_2' = \frac{\Delta_2}{A} = \frac{20}{12} = \frac{10}{6} = \frac{5}{3}$$

$$I_1' = 3.33A \quad I_2' = \frac{5}{3} = 1.66A$$

$$I_3' = I_1' - I_2' = 3.33 - 1.66 = 1.67$$

When 5V source acting alone

Apply KVL in loop ①.

$$2I_1' + 2(I_1' - I_2') = 0.$$

$$4I_1' - 2I_2' = 0 \rightarrow \text{eq. ①}$$

Apply KVL in loop ②.

$$-5 + 2I_2' + 2(I_2' - I_1') = 0.$$

$$-5 + 4I_2' = 5 \rightarrow \text{eq. ②}$$

$$\begin{bmatrix} 4 & -2 \\ -2 & 4 \end{bmatrix} \begin{bmatrix} I_1' \\ I_2' \end{bmatrix} = \begin{bmatrix} 0 \\ 5 \end{bmatrix}$$


$$I_1'' = \frac{41}{A} \quad I_2'' = \frac{42}{A}$$


$$A = \begin{vmatrix} 0 & -2 \\ 5 & 4 \end{vmatrix} \quad A = \begin{vmatrix} 4 & 0 \\ -2 & 5 \end{vmatrix}$$

$$\Delta_1 = (0 + 10) \quad \Delta_2 = (20 - 0) \quad A = 16 - 4 = 12$$

$$A = 10 \quad \Delta_2 = 20 \quad A = 12$$
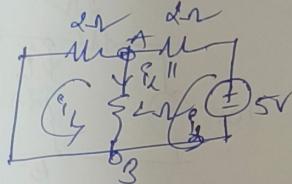
$$I_1'' = \frac{10}{12} = 0.833A \quad I_2'' = \frac{20}{12} = \frac{10}{6} = 1.66A$$




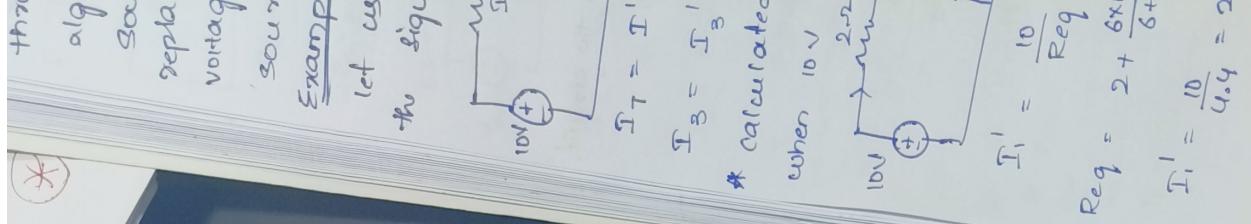

$$i_2'' = i_2' - i_1' = 1.667 - 0.834 = 0.834$$

$$i_L = i_L' + i_L'' = 1.667 + 0.834 = \underline{\underline{2.5 \text{ A}}}$$

When two sources acting

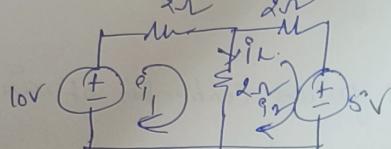

Apply KVL to loop 1

$$-10 + 4i_1 + 2(i_1 - i_2) = 0.$$

$$4i_1 - 2i_2 = 10 \rightarrow \text{eq } ①$$

Apply KVL in loop 2

$$2(i_2 - i_1) + 2i_2 + 5 = 0.$$

$$-2i_1 + 4i_2 = -5 \rightarrow \text{eq } ②$$

$$\begin{pmatrix} 4 & -2 \\ -2 & 4 \end{pmatrix} \begin{pmatrix} i_1 \\ i_2 \end{pmatrix} = \begin{pmatrix} 10 \\ -5 \end{pmatrix}$$

$$i_1 = \frac{A_1}{A} \quad i_2 = \frac{A_2}{A}$$

$$A_1 = \begin{vmatrix} 10 & -2 \\ -5 & 4 \end{vmatrix} \quad A_2 = \begin{vmatrix} 4 & 10 \\ 2 & -5 \end{vmatrix}$$

$$A_1 = 40 - 10 = 30$$

$$A_2 = -20 + 20 = 0.$$

$$A = \begin{vmatrix} 4 & -2 \\ -2 & 4 \end{vmatrix}$$

$$A = 16 - 4 = 12$$

$$i_1 = \frac{A_1}{A} = \frac{30}{12} = 2.5 \text{ A}$$

$$i_1 = 2.5 \text{ A}$$

$$i_2 = \frac{A_2}{A} = \frac{0}{12} = 0 \text{ A}$$

$i_L = 2.5 + 0 = \underline{\underline{2.5 \text{ A}}}$  Hence proved.

through  
 dependent  
 source  
 replaced  
 Voltage  
 sources  
Example:  
 left as is  
 $\rightarrow R_0$  square

$$T_1 = T_1' +$$

$$T_2 = T_2' +$$


\* saturated  
when 10 V  
2 ohm  
10V

$$T_1' = \frac{10}{R_1}$$

$$T_2' = \frac{10}{R_2}$$


Q. a. Determine equivalent resistance for the circuit shown

In fig.

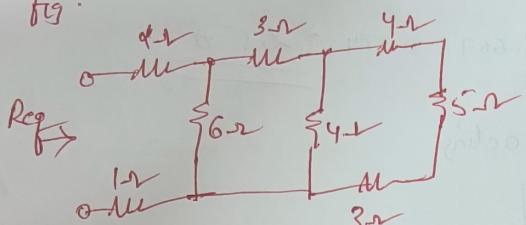


(6n)

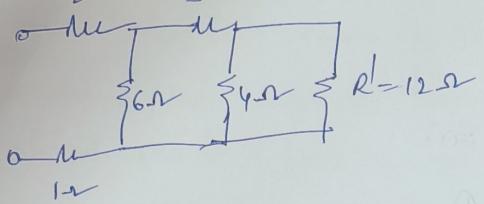
Sol:- Reduce the network using series parallel combination of resistance




$$R^1 = 4 + 5 + 3 = 12 \Omega$$

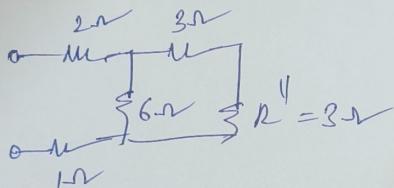
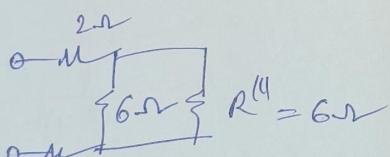
$$R^{II} = \frac{12 \times 4}{12 + 4} = \frac{48}{16} = 3 \Omega$$



$$R^{III} = 3 + 3 = 6 \Omega$$

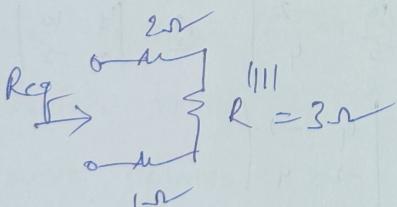

$$R^{IV} = \frac{6 \times 6}{6 + 6} = \frac{36}{12} = 3 \Omega$$

$$R_{eq} = 2 + 3 + 4 = 6 \Omega$$


## (\*) Maximum power Transfer theorem

→ This theorem is used to find the value of load resistance for which there would be maximum amount of power transfer from source to load.

### Statement

"A resistance load, being connected to a dc network receives maximum power when the load resistance is equal to the internal resistance (Thévenin's equivalent resistance) of the source network as seen from the load terminals."

### Explanation

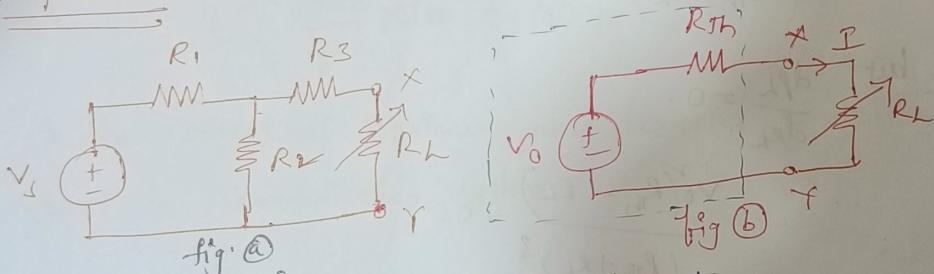

A variable resistance  $R_L$  is connected to a dc source network as shown in fig. (a) while fig (b) represents the Thévenin voltage  $V_0$  and Thévenin Resistance  $R_{th}$  of the source network.

$$\text{With reference to fig (b)} \quad I = \frac{V_0}{R_{th} + R_L}$$

while the power delivered to the resistive load is

$$P_L = I^2 R_L = \left( \frac{V_0}{R_{Th} + R_L} \right)^2 \times R_L$$

$P_L$  can be maximised by varying  $R_L$  and hence maximum power can be delivered when  $\frac{dP_L}{dR_L} = 0$

However

$$\begin{aligned} \frac{dP_L}{dR_L} &= \frac{1}{\left( R_{Th} + R_L \right)^2} \cdot 2 \left[ (R_{Th} + R_L)^2 \frac{d}{dR_L} (V_0^2 R_L) - V_0^2 R_L \frac{d}{dR_L} (R_{Th} + R_L)^2 \right] \\ &\Rightarrow \frac{1}{(R_{Th} + R_L)^4} \left[ (R_{Th} + R_L)^2 V_0^2 - V_0^2 R_L + 2 [R_{Th} + R_L] \right] \\ &= \frac{V_0^2 (R_{Th} + R_L - 2R_L)}{(R_{Th} + R_L)^3} = \frac{V_0^2 R_{Th} - R_L}{(R_{Th} + R_L)^3} \end{aligned}$$

but  $\frac{dP_L}{dR_L} = 0$ .

$$\therefore \frac{V_0^2 (R_{Th} - R_L)}{(R_{Th} + R_L)^3} = 0.$$

which gives  $R_{Th} - R_L = 0 \quad (0)$

$$\boxed{R_{Th} = R_L} \rightarrow \text{Condition for maximum power transfer}$$

Hence, it has been proved that power transfer from a dc source network to a resistive network is maximum when the internal resistance of the dc source network is equal to the load resistance.

When  $R_{Th} = R_L$  the system being perfectly matched for load and source, the source power transfer becomes maximum and thus amount of power ( $P_{max}$ ) can be obtained as

$$P_{max} = \frac{V_o^2 R_{Th}}{(R_{Th} + R_{Th})^2} = \frac{V_o^2}{4 R_{Th}}$$

Obviously the power Transfer by the source would be

also  $\frac{V_o^2}{4 R_{Th}}$ , the load power and source power being same.


To find power supplied is  $P = 2 \frac{V_o^2}{4 R_{Th}} = \frac{V_o^2}{2 R_{Th}}$

During Maximum power transfer the efficiency becomes

$$\eta = \frac{P_{max}}{P} \times 100 = 50\%$$


→ The concept of maximum power transfer is mainly used in communication systems.

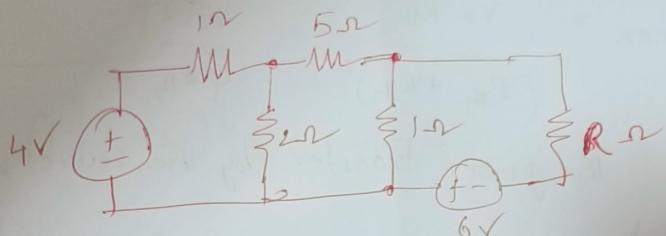★ Find the value of  $R$  in the circuit of fig. such that maximum power transfer takes place. What is the amount of this power.



Q:- Let the  $R$  be replaced first and the open circuit

voltage be  $V_{oc}$

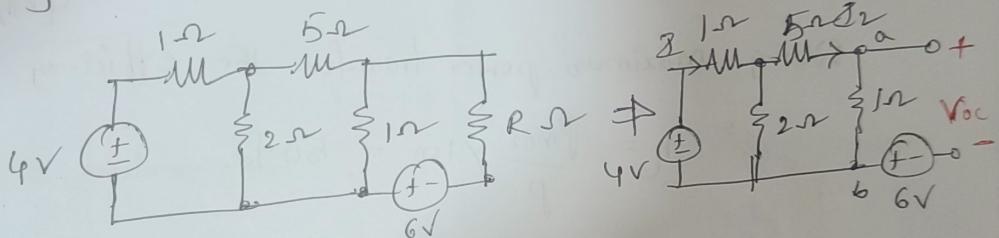

$$\text{Here } I = \frac{4V}{[(5+1)||2]+1} = \frac{4}{5||2} = \frac{8}{15} A$$

$$\therefore I_2 = I \cdot \frac{2}{2+5+1} = \frac{8}{5} \times \frac{1}{4} = \frac{2}{5} A.$$

The drop across ab branch is then

$$V_{ab} = \frac{2}{5} \times 1 = \frac{2}{5} V$$

Obviously

$$V_{oc} = V_{ab} + 6 = \frac{2}{5} + 6 = \frac{32}{5} V.$$

$$V_{oc} = 6.4 \text{ Volts}$$

When  $R_{th} = R_L$  the system being perfectly matched for load and source, the source power transfer becomes maximum and this amount of power ( $P_{max}$ ) can be obtained as

$$P_{max} = \frac{V_o^2 R_{th}}{(R_{th} + R_{th})^2} = \frac{V_o^2}{4 R_{th}}$$

Obviously the power transfer by the source would be

also  $\frac{V_o^2}{4 R_{th}}$ , the load power and source power being


same. Total power supplied is  $P = 2 \frac{V_o^2}{4 R_{th}} = \frac{V_o^2}{2 R_{th}}$

During Maximum power transfer the efficiency becomes

$$\eta = \frac{P_{max}}{P} \times 100 = 50\%$$

→ The concept of Maximum power transfer is mainly used in communication systems.

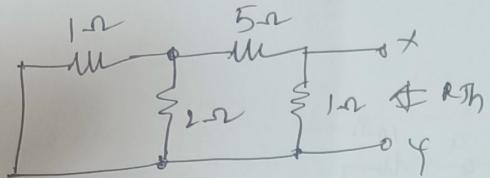To find the internal resistance of the circuit across X-Y with reference to fig (b)




$$\begin{aligned}
 R_{Th} &= (1 \parallel 2 + 5) \parallel 1 = \cancel{\left( \frac{1}{1+2} + 5 \right)} \parallel 1 \\
 &= \left[ \left( \frac{1 \times 2}{1+2} \right) + 5 \right] \parallel 1 \\
 &= \frac{\frac{17}{3} \times 1}{\frac{17}{3} + 1} = \frac{17}{20} = 0.85 \Omega
 \end{aligned}$$

Or per maximum power transfer theorem  $R_{Th} = R_L = 0.85 \Omega$


$$\text{Maximum power } P_{max} = \frac{V_{oc}^2}{4R_{Th}} = \frac{(6.4)^2}{4 \times 0.85} = \underline{\underline{12 W}}$$

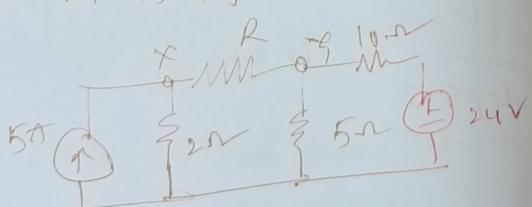Q) What should be the value of R such that maximum power transfer takes place from the rest of the network to R in fig. Obtain the amount of this power.



(\*) Assuming Maximum Power Transfer  
R<sub>L</sub> find the value.

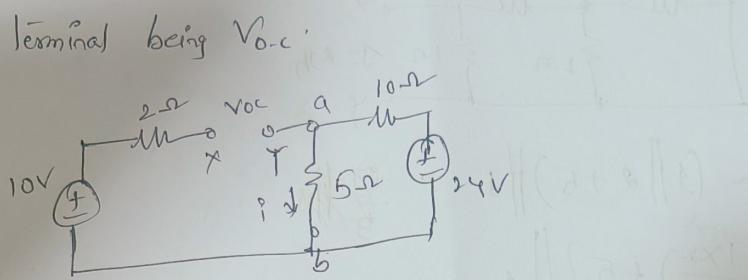Sol: Let first convert the 'A' source to 'V' source  
and remove R from X-Y terminal, the voltage at these  
terminal being V<sub>oc</sub>.




$$\therefore V_{ab} = \text{drop across } 5\Omega = 16 \times 5 = 8V$$

thus in the left loop  $-10 + V_{oc} + 8 = 0$ .

$$V_{oc} = 2 \text{ Volts}$$

With reference to R<sub>th</sub> (internal resistance looking through  
X-Y) is obtained as

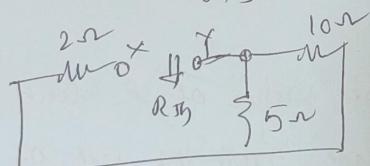
$$R_{th} = \frac{10 \times 5}{10 + 5} + 2 = 5.33 \Omega$$



As per maximum power transfer  $R = R_{th} = 5.33 \Omega$

$$P_{max} = \frac{V_{oc}^2}{4R} = \frac{2^2}{4 \times 5.33} = 188 \text{ mW.}$$

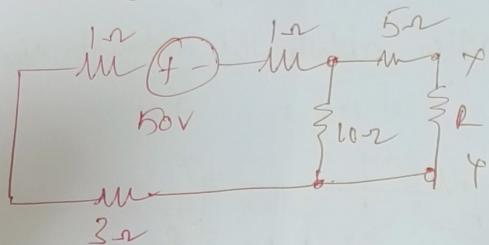Assuming Maximum power transfer from the source to R, find the value of the amount of power in the circuit of fig.




Sol:- R is removed by open circuit. With reference to fig.

$$I = \frac{50}{1+1+3+10} = \frac{50}{15} = 3.33 \text{ A}$$

$$\therefore V_{oc} = V_{10\Omega} = 3.33 \times 10 = 33.33 \text{ V}$$


It may be noted that b may be positive polarity as the current in 10Ω resistor flows from b to a
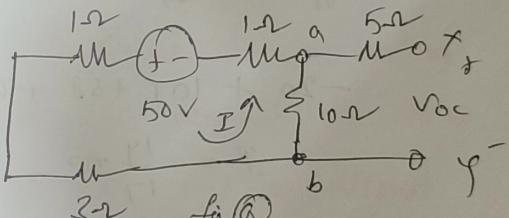
$$\therefore V_{x-y} = -33.33 \text{ V} = V_{oc}$$



With reference to fig. (b)
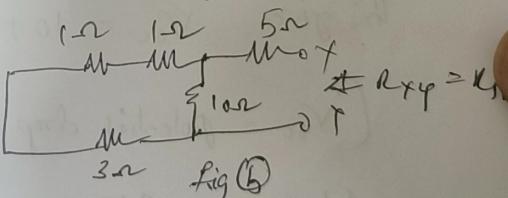
$$R_{Th} = \frac{5 \times 10}{5+10} + 5 = 8.33 \Omega$$




As per maximum power transfer theorem


$$R = R_{Th} = 8.33 \Omega$$

$$P_{max} = \frac{V_{oc}^2}{4R} = \frac{(33.33)^2}{4 \times 8.33} = 33.34 \text{ Watts}$$

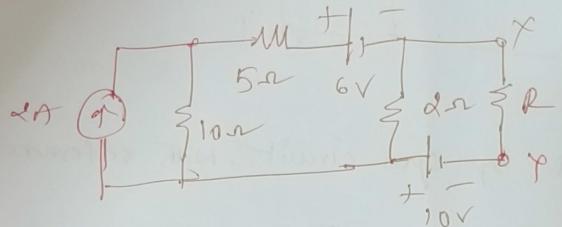Q1) Find R to have maximum power transfer to the circuit of fig. Also obtain the amount of maximum power.



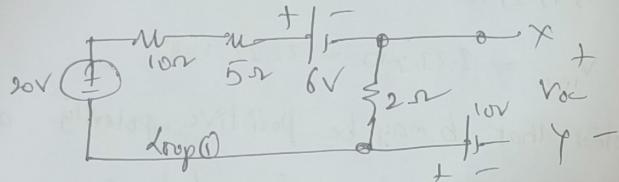Sol:- let us first convert current source to voltage source



The application of mesh analysis is left loop (or loop 1).

$$-20 + 10I + 5I + 6 + 2I = 0.$$


$$I = \frac{14}{17} A$$

this gives  $V_{oc} = 10 + \frac{14}{17} \times 2 = 11.65 V$

( $V_{oc}$  = Potential drop across  $2\Omega$  + Potential of  $10V$  battery)

The internal resistance of the circuit looking from X-Y terminals is
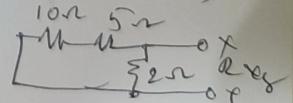
$$R_{in} = \frac{15 \times 2}{15+2} = \frac{30}{17} = 1.765 \Omega$$



As per Thévenin's maximum power transfer

$$R = 1.765 = R_{Th}$$

$$P_{max} = \frac{V_{Th}^2}{4R} = \frac{11.65^2}{4 \times 1.765} = \underline{\underline{19.22 \text{ W}}}$$

Ques: The open circuit voltage of a standard car battery is 12.6 V and the short circuit current is approximately 300 A. What is the available power from the battery.

Sol:-

$$R_{oc} = \frac{V_{oc}}{I_{sc}} = \frac{12.6}{300} = 0.042 \Omega$$

$$P_{ave} = \frac{V_{Th}^2}{4R_{th}} = \frac{V_{oc}^2}{4R_{oc}} = \frac{(12.6)^2}{4 \times 0.042} = \underline{\underline{94.5 \text{ W}}}$$

Ques: A stereo sound system is operated from a battery which is made from 8 dry cells connected in series. Each cell has an emf of 1.5 V and an internal resistance of 0.75 Ω. How much is the available power from this battery.

Sol:-


$$V_{oc} = 8 \times 1.5 = 12 \text{ V}$$

$$\text{Output Impedance } R_o = 8 \times 0.75 = 6 \Omega$$

$$P_{max} = \frac{V_{oc}^2}{4R_o} = \frac{(12)^2}{4 \times 6} = \underline{\underline{6 \text{ W}}}$$
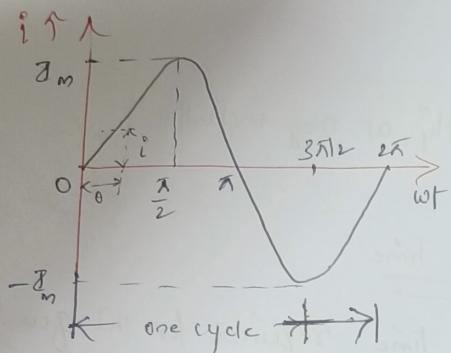
## (\*) Alternating voltage and currents and their Mathematical Relation and graphical representation


→ In AC power the voltages and currents vary with time sinusoidally. Such a variation is shown graphically in fig -



Current  $i$  vs angle  $\omega t$

Mathematically


$$i = I_m \sin \omega t$$

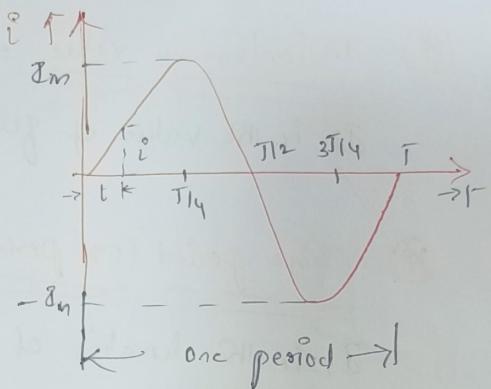

current  $i$  vs  $t$
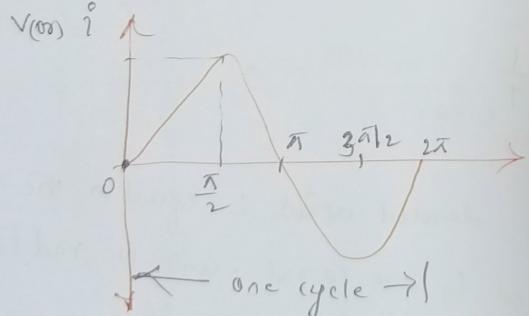
### Terminology

Cycle : One complete set of positive and negative values of the function is called a cycle.



④ Maximum Value or peak value

If it is the maximum value ( $E_m$ ) or positive or negative of the quantity. It is also sometimes called amplitude of the sinusoid.

⑤ Instantaneous Value :

If it is the value of quantity at any instant.

⑥ Time period (or) Periodic Time

If it is the duration of the time required for the quantity to complete one cycle. It is denoted by  $T$ .

⑦ Frequency

If it is the no. of cycles that occur in one second. It is denoted by  $f$ . The unit of frequency is hertz (Hz) which is same as cycles/second. Obviously frequency is reciprocal of time period.

$$f = \frac{1}{T}$$


⑧ Angular frequency

Angular frequency denoted as ' $\omega$ ' is equal to the number of radians covered in one second. Unit is rad/sec.

$$\omega = 2\pi f \quad (or) \quad \omega = \frac{2\pi}{T}$$

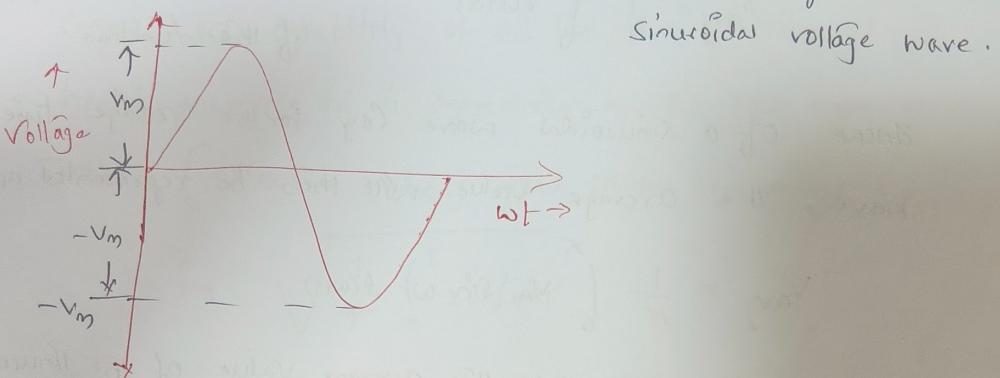
### Peak value (Amplitude)

If  $V$  is the maximum value of the wave during either positive or negative half cycle.  $V_m$  is the peak value of sinusoidal voltage wave.


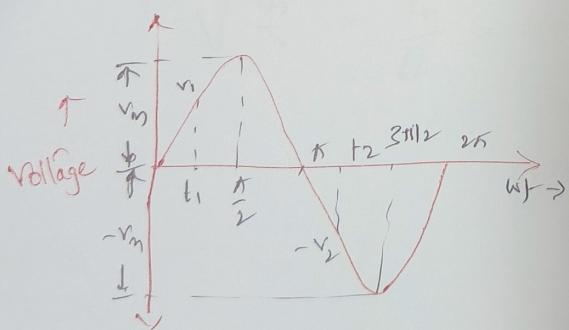
### Instantaneous value

If  $v$  is the value of sinewave at any instant of the cycle. This value is different points along the wave form. In fig.  $v_1$  is the instantaneous value of time  $t_1$  and  $-v_2$  is the instantaneous value of time  $t_2$ .





## Rms value (Root Mean square value)

As the effective value of a sine wave is zero for the entire cycle hence in order to get the effective value, we

compute the capability of the sine wave in terms of its heating power. This is represented by the root mean square value [effective value] and can be represented by

$$V_{rms} = \sqrt{\frac{1}{T} \int_0^T V(t)^2 dt}$$

for a periodic function, T being the time period.

Hence for a sinusoidal voltage waves.

$$\begin{aligned} V_{rms} &= \sqrt{\frac{1}{2\pi} \int_0^{2\pi} (V_m \sin \omega t)^2 d(\omega t)} \\ &= \sqrt{\frac{1}{2\pi} \int_0^{2\pi} V_m^2 \left[ \frac{1 - \cos 2\omega t}{2} \right] d(\omega t)} \\ &= \sqrt{\frac{V_m^2}{2}} = \frac{V_m}{\sqrt{2}} = 0.707 V_m \end{aligned}$$

 A voltage wave is represented by  $V = 200 \sin 314t$

Find (a) Maximum value (b) RMS value (c) Average value

(d) Frequency (e) Time period (f) Instantaneous value

after 0.05 sec.

Sol:- Gives  $V = 200 \sin 314t$

(a) from above peak value (or) maximum value is  $200\text{V}$  ( $V_m$ )

(b) RMS value is

$$V = \frac{V_m}{\sqrt{2}} = 141.4\text{V}$$

(c) Average value is

$$V_{avg} = \frac{2V_m}{\pi} = 0.637 V_m = 127.4\text{V}$$

(d) Frequency ( $f$ ) =  $\frac{\omega}{2\pi} = \frac{314}{2\pi} = 50\text{Hz}$

(e) Time period  $T = \frac{1}{f} = 0.02\text{sec}$ .

(f) Instantaneous value of the given wave after 0.05 sec

$$V = 200 \sin (314 \times 0.05) = \underline{\underline{54.12\text{V}}} = 54.12\text{V}$$

(F)

### Form factor

The ratio of effective value to the average value is known as the form factor of waveform.

$$\text{Form factor} = \frac{\text{Rms value}}{\text{Average value}}$$

(\*)

### Peak factor or Crest factor or amplitude factor

The ratio of peak value to rms value is known as peak factor.

$$\text{Peak factor} = \frac{\text{Peak or maximum value}}{\text{Rms value.}}$$

### Average Value

In general the average value of a periodic function  $x(t)$  can be represented as

$$x_{\text{avg}} = \frac{1}{T} \int_0^T x(t) dt \quad \text{where } T \text{ is the time period of the function.}$$

In case of a sinusoidal wave say for the voltage time wave, the average value will then be represented as

$$V_{\text{avg}} = \frac{1}{\pi} \int_0^{\pi} V_m \sin \omega t d(\omega t)$$

It may be noted that the average value of the sinusoidal voltage wave is computed for  $\frac{1}{2}$  cycle as the average value of the sine wave would be zero for a complete cycle.

$$V_{\text{avg}} = \frac{1}{\pi} \left[ -V_m \cos \omega t \right]_0^{\pi}$$

$$= \frac{2V_m}{\pi} = 0.637 V_m$$

of?