






School of Engineering

Question Bank

I Year B. Tech – I Semester – 2023-24

Basic Electrical And Electronics Engineering

(MR23-1ES0101)

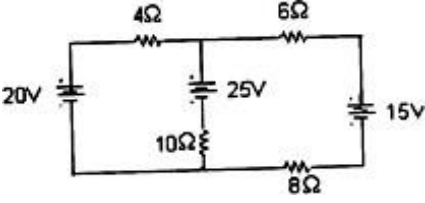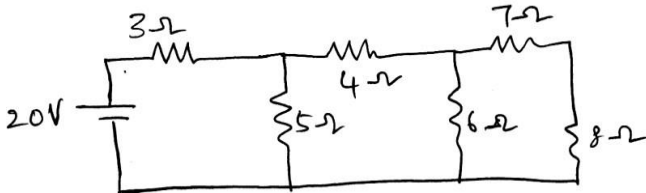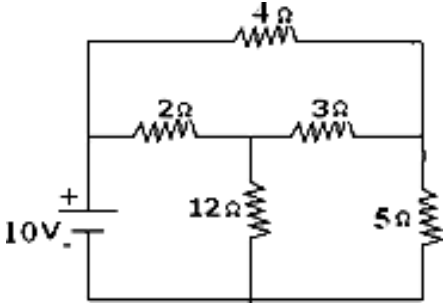Q. No	Question	Course Outcome	Question Level	Marks	Section	Unit
1	<p>a) State and explain Kirchhoff's laws. b) By applying Kirchhoff's law, find the power across each of the elements in the circuit as shown in the figure</p> 	CO1	Easy	4 4	Section- I	1
2	<p>a) Explain about different types of sources. b) Find the power dissipated in the 4Ω resistor of the following circuit shown below. Use mesh analysis.</p> 	CO1	Medium	4 4	Section- I	1
3	<p>Find the current supplied by 10V battery for the following network shown in figure by using mesh analysis.</p> 	CO1	Complex	8	Section- I	1






4	<p>Calculate the equivalent resistance across terminals P and Q for the network shown below.</p>	CO1	Complex	8	Section-I	1
5	<p>a) Find the equivalent resistance across X, Y</p> <p>terminals of figure below.</p> <p>b) Using delta to star transformation, determine the resistance between terminals a and b and the total power drawn from the supply in the circuit for the following figure.</p>	CO1	Medium	4 4	Section-I	1
6	<p>Determine the current flowing through 15 Ω, 30 Ω and 40 Ω resistors if the applied DC voltage is 220 V. Also find power dissipated in 10 Ω resistor shown in figure.</p>	CO1	Easy	8	Section-I	1





7	Three equal resistors each of R ohms are connected in delta. Derive the value of resistors in equivalent star.	CO1	Easy	8	Section- I	1
8	Find the equivalent resistance between two points x, y of figure shown below. 	CO1	Medium	8	Section- I	1
9	<p>a) State and explain Thevenin's theorem.</p> <p>b) Calculate V_X in the circuit shown in below figure.</p>	CO2	Easy	4 4	Section- II	2
10	<p>Solve network shown in below Figure using Thevenin's equivalent circuit and find current through 2 ohms resistor.</p>	CO2	Easy	8	Section- II	2

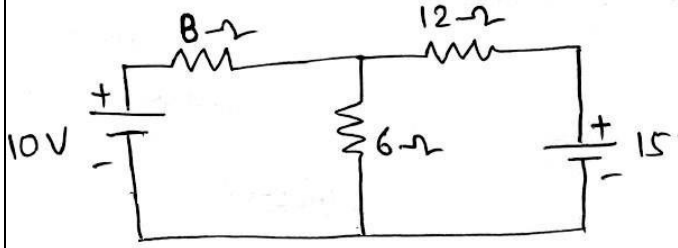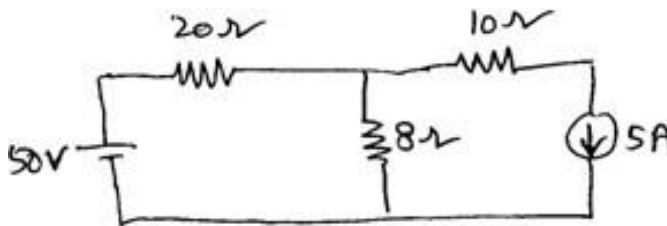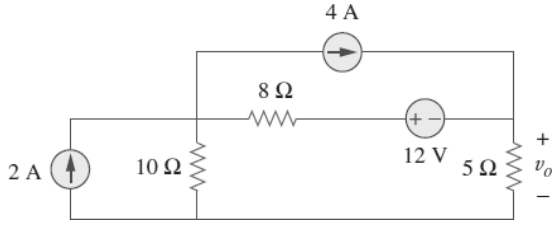

11	<p>a) State and Explain Superposition theorem. b) Using superposition theorem, determine the current through 12-ohm resistor shown in following figure.</p> 	CO2	Medium	44	Section- II	2
12	<p>Using superposition theorem, find the current through the 8 Ω resistor, as shown in below figure.</p> 	CO2	Complex	8	Section- II	2
13	<p>Find v_o using superposition theorem in the circuit shown in figure below.</p> 	CO2	Complex	8	Section- II	2

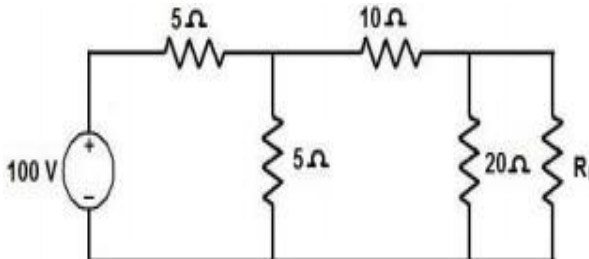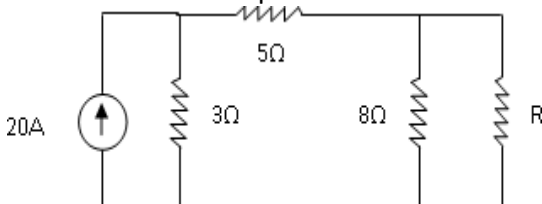

14	Find the value of R_L so that maximum power is delivered to the load resistance and also find the maximum power delivered for the figure shown below. 	CO2	Medium	8	Section- II	2
15	In the circuit as shown in following figure , maximum power is absorbed by the resistance R. Compute the value of R and the value of maximum power consumed. 	CO2	Medium	8	Section- II	2
16	Define RMS value and Average value of an alternating quantity. Determine these values for a half wave rectified sine wave.	CO2	Easy	8	Section- II	2
17	a) Derive an emf equation of a single-phase transformer. b) A 30 KVA single phase transformer has 500 turns on primary and 60 turns on secondary winding. The primary is connected to 300 volt, 50Hz supply. Find the full load primary and secondary currents, secondary emf and the maximum flux in the core. Neglect leakage drop and no-load current.	CO3	Easy	4 4	Section- III	3
18	a) How a Single-phase transformer works? Explain. b) A 2200/220 V, 50Hz single phase transformer has emf per turn of approximately 10 V. Calculate a) the number of primary and secondary turns b) the cross-sectional area of the core if the maximum flux density is limited to 1.5 T.	CO3	Easy	4 4	Section- III	3
19	Explain working Principle and operation of DC motor.	CO3	Medium	8	Section- III	3



20	a) Derive EMF equation of DC generator. b) Derive the Torque equation of DC motor.	C03	Easy	4 4	Section- III	3
21	Explain the Constructional details of DC generator.	C03	Medium	8	Section- III	3
22	Explain about the construction of single-phase Transformer.	C03	Easy	8	Section- III	3
23	a) Explain the applications of stepper motor in detail. b) Explain the applications of Induction motor in detail.	C03	Complex	4 4	Section- III	3
24	Explain the applications of BLDC motor in detail.	C03	Easy	8	Section- III	3
25	Illustrate the operation Zener diode and explain its V – I characteristics.	C04	Easy	8	Section- IV	4
26	Draw the forward and reverse characteristics of a p-n junction diode and explain them.	C04	Medium	8	Section- IV	4
27	a) Explain the operation of Center-tapped full wave rectifier with relevant waveforms. b) Derive expression for ripple factor for a full wave rectifier.	C04	Medium	4 4	Section- IV	4
28	Explain the operation of Half Wave Rectifier with necessary waveforms.	C04	Easy	8	Section- IV	4
29	Compare Half wave rectifier and Full wave rectifier in any four aspects.	C04	Easy	8	Section- IV	4
30	Explain the construction and principle of operation of NPN transistor with neat diagram.	C04	Medium	8	Section- IV	4
31	Explain the construction and principle of operation of PNP transistor with neat diagram.	C04	Medium	8	Section- IV	4
32	a) Explain the Classification of batteries for Electric Vehicle (Lithium-Ion) b) Explain the Applications of various batteries for Electric Vehicle (Lithium-Ion)	C04	Complex	4 4	Section- IV	4
33	Perform the following conversions $(476.64)_{10} = ()_2 = ()_8$	C05	Easy	8	Section- V	5
34	a) Convert $(946)_{10}$ into Hexadecimal. b) Find X for the following conversion $(367)_8 = (x)_2$	C05	Medium	4 4	Section- V	5
35	Solve for x for the following $(B9F.AE)_{16} = (x)_8 = (x)_{10}$	C05	Medium	8	Section- V	5
36	Express the following numbers into decimal: $(10110.0101)_2$, $(16.5)_{16}$, $(26.24)_8$.	C05	Medium	8	Section- V	5
37	Explain various number systems and their	C05	Medium	8	Section- V	5



MALLA REDDY UNIVERSITY

(Telangana State Private Universities Act No. 13 of 2020 &
G.O.Ms.No.14, Higher Education (UE) Department)

Maisammaguda, Kompally,
Medchal - Malkajgiri
District Hyderabad - 500100,
Telangana

	conversion with examples for each.					
38	Explain about AND, OR, NOT, NAND, NOR and EX-OR gates in detail.	C05	Medium	8	Section- V	5
39	a) Perform the following arithmetic using 2's complement method. i) 101111-100110 ii) 111001-011010 b) Convert the given gray code number to equivalent binary 001001011110010.	C05	Complex	4 4	Section- V	5
40	Convert the given Octal number (61234.03) ₈ to Hexadecimal Number and Decimal Number.	C05	Easy	8	Section- V	5